

TI Precision Labs – Motor Drivers

Presented and Prepared by Sanmeshkumar Udhayakumar






Easy model of BLDC motor


Permanent magnet rotor

Stationary coils on stator

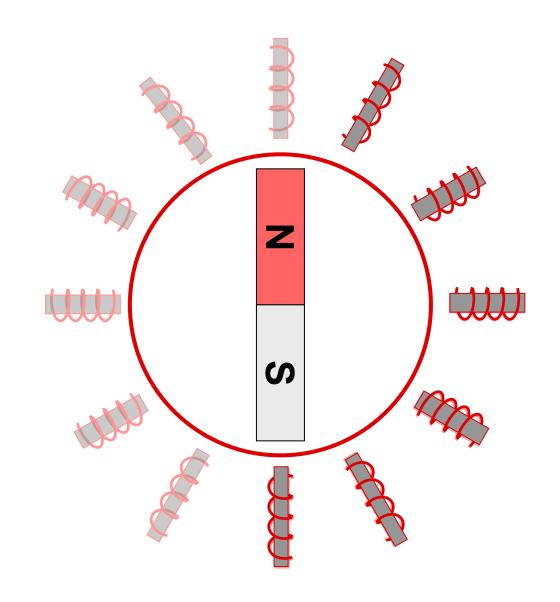Moving magnetic field continuously drags the rotor along the circle




BLDC commutation

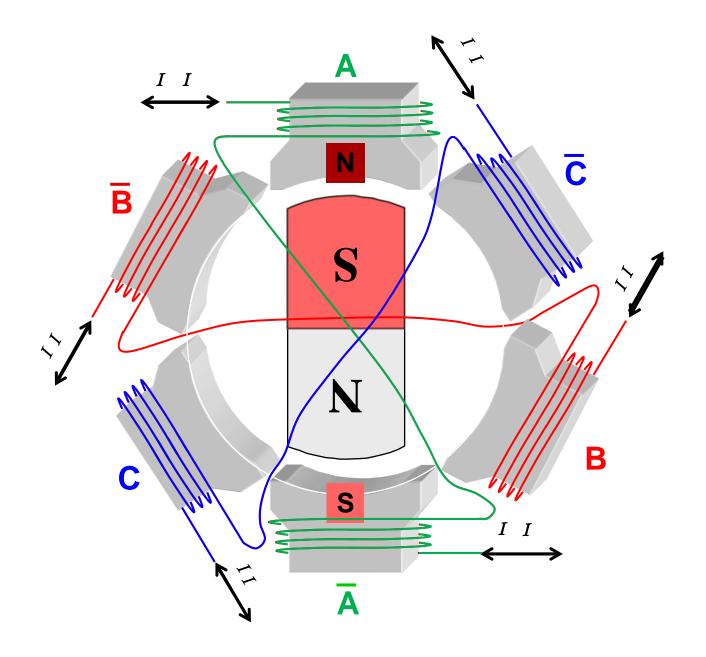


Brushed vs brushless DC motor

Brushed-DC motor

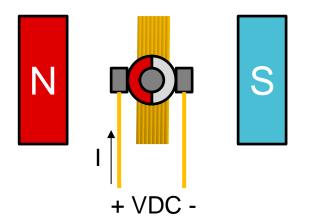

Brushless-DC motor

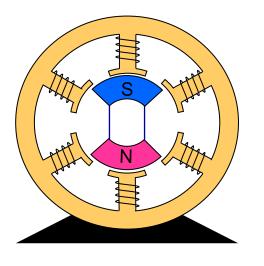


Commutation automatically handled by mechanical design


Motor driver circuitry needs to handle commutation

Motor winding configuration

Wye (Y) winding star connection

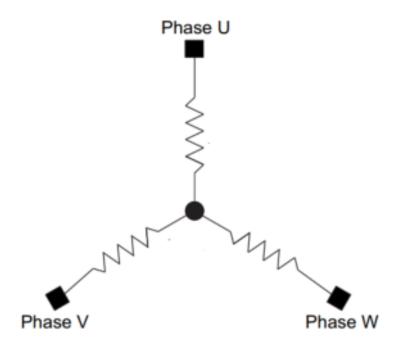



Delta (Δ) winding connection

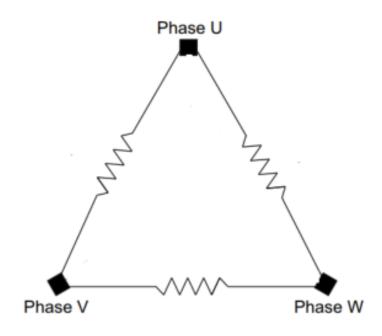

Both are driven the same way

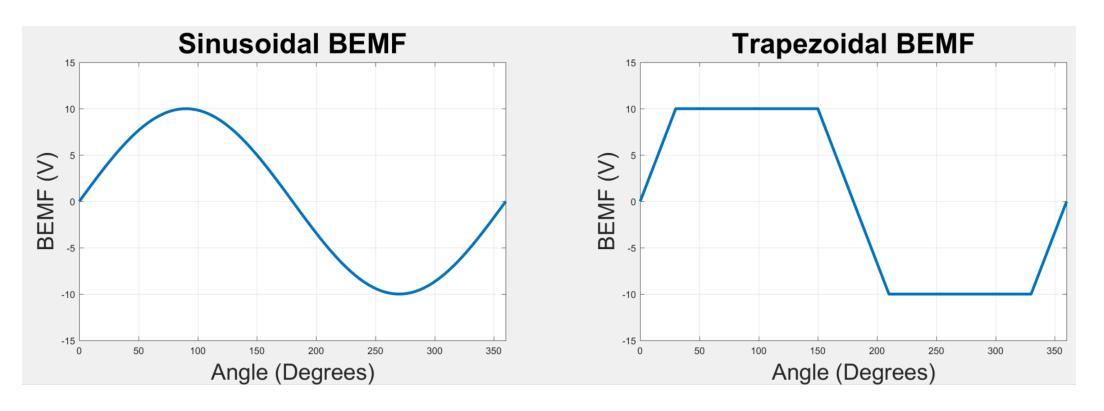Sinusoidal vs trapezoidal back-electromotive force (BEMF)



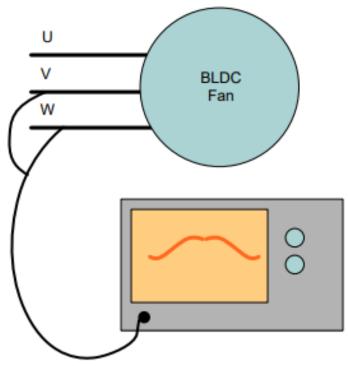


Electrical vs mechanical cycle

Mechanical cycle:

Time for the motor to travel one full revolution




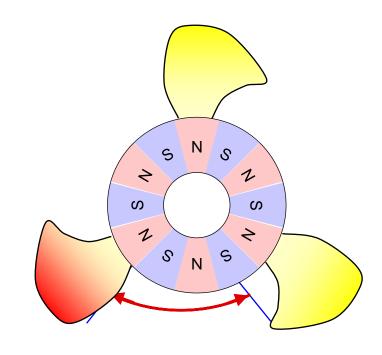Time for the rotor to pass a pair of poles.




$$mechanical\ speed = \frac{electrical\ speed}{\#\ of\ pole\ pairs}$$


Motor control circuitry

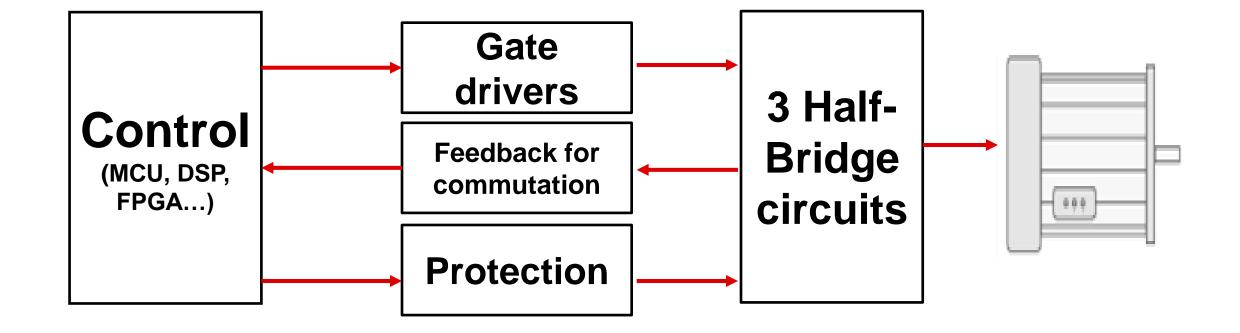

3 Half-Bridge circuits and gate drivers

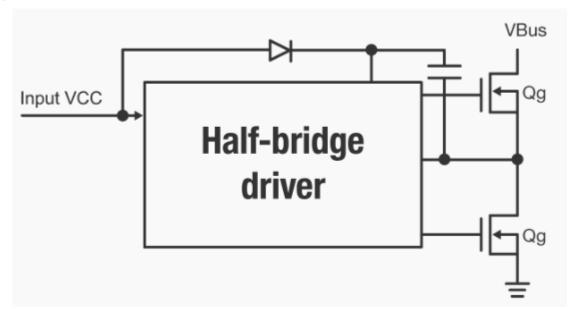
- 3 Half-bridge circuits indicated by dotted boxes
- Half-bridge circuits connect motor phases to Vcc or GND
- Gate drivers turn on/off MOSFETs in half-bridge circuits to connect to Vcc or GND



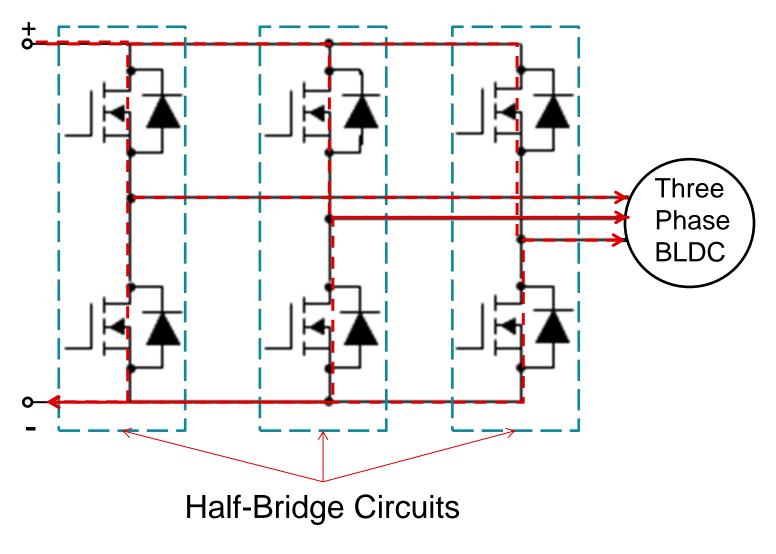


Control Block

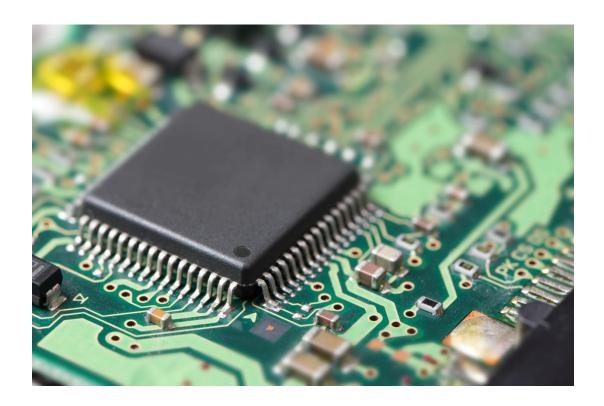
- Control block: Controls gate drivers to dictate commutation through the halfbridge circuits
 - MCU
 - FPGA
 - DSP
 - Digital state machine
 - Pure analog implementation




Feedback for Commutation

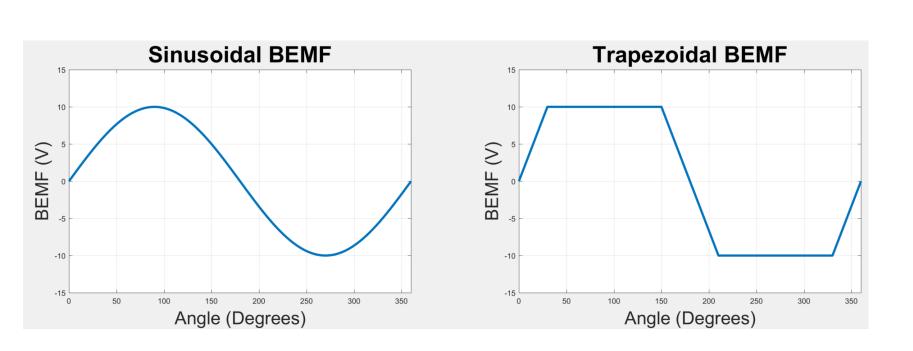- Feedback of rotor position for commutation:
 - Encoders
 - Hall-effect
 - BEMF



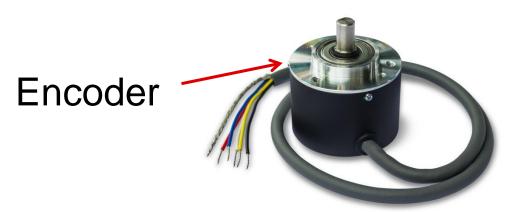

Hall-Effect Sensors

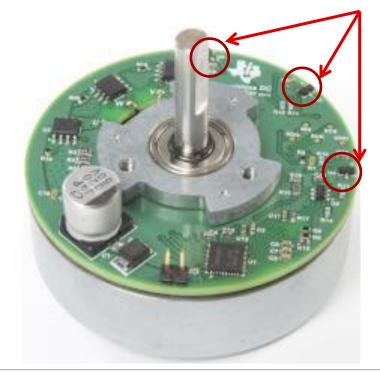

Motor Circuitry Protection

Over current protection (OCP)

Thermal shutdown

Under-Voltage lock-out (UVLO)

Shoot-Through

Lock detect

Anti-Voltage surge (AVS)

To find more motor driver technical resources and search products, visit ti.com/motordrivers